



**Department of Computer Science & Engineering (CSE)**  
**School of Engineering, Technology & Sciences**  
**INDEPENDENT UNIVERSITY, BANGLADESH (IUB)**

**Course Title:** Electronics I  
**Course Code:** CSE210  
**Section:** 01

SUBMITTED FROM

**Student Name:** MD. Rayhan Hossain  
**Student ID:** 2211229  
**Serial no:** 11  
**Submission Date:** 29/08/2024

SUBMITTED TO

**Faculty Name:** Noushin Anan

### Example 3.1

(a) So,  $I_C \cong I_E$   
 $\therefore I_C = 3 \text{ mA}$

Here  
 $I_E = 3 \text{ mA}$   
 $V_{CE} = 10 \text{ V}$

(b) So,  $I_C \cong I_E$   
 $\therefore I_C = 3 \text{ mA}$

Here,  
 $I_E = 3 \text{ mA}$   
 $V_{CE} = 2 \text{ V}$

(c) From the figure 3.7 the curve of  $V_{CE} = 20 \text{ V}$  and the point when  $I_C$  (y-axis) is  $4 \text{ mA}$  the x-axis  $V_{BE}$  (x-axis) point approximately  $0.73 \text{ mA}$

Here  
 $I_C = 4 \text{ mA}$   
 $V_{CE} = 20 \text{ V}$

(d) From the figure 3.10(c) it an simplified ~~the~~ curve with value of  $0.7 \text{ V}$   ~~$V_{BE}$~~   $V_{BE}$ . So, for any value of  $I_C$  and  $V_{CE}$   $V_{BE}$  remain same  $0.7 \text{ V}$

Here  
 $I_C = 4 \text{ mA}$   
 $V_{CE} = 20 \text{ V}$

### Example 3.2

(a) So, From the 3.13(a) when  $I_B = 30 \mu\text{A}$  and  $V_{CE} = 10 \text{ V}$  (x-axis) the  $I_C$  (y-axis) value approximately  $3.2 \text{ mA}$

Here  
 $I_B = 30 \mu\text{A}$   
 $V_{CE} = 10 \text{ V}$

(b) From 3.13(b)  $V_{CE} = 15 \text{ V}$  between 10 to 20 V and  $V_{BE} = 0.7$  So,  $I_B = 20 \mu\text{A}$

Here  
 $V_{CE} = 15 \text{ V}$   
 $V_{BE} = 0.7 \text{ V}$

Now in 3.13(a)  $I_B = 20 \mu\text{A}$  and  $V_{CE} = 15 \text{ V}$



So  $I_C = 2.25 \text{ mA}$  approximately

### Exercise 11

From Figure 3.8  
 $I_C \approx I_E$   
 $\therefore I_C = 5 \text{ mA}$

Here,

$$I_E = 5 \text{ mA}$$

$$V_{CB} = 1, 10, 20 \text{ V}$$

From figure 3.7

$$I_E = 5 \text{ mA} \text{ always}$$

So, when  $V_{CB} = 1 \text{ V}$

$$V_{BE} = 0.8 \text{ V}$$

$$V_{CB} = 10 \text{ V}$$

$$V_{BE} = 0.78 \text{ V}$$

$$V_{CB} = 20 \text{ V}$$

$$V_{BE} = 0.76 \text{ V}$$

In the figure 3.7 there are three curve lines for  $V_{CB} 1 \text{ V}, 10 \text{ V}$  &  $20 \text{ V}$ . and for  $I_E$  fixed ( $5 \text{ mA}$ )  $V_{BE}$  have three different value but close enough. So we can say that in  $V_{BE}$  and  $I_E$  relationship graph  $V_{CB}$  has slight effect.

### Exercise 12

① average ac resistance,  $r_{av} = \frac{\Delta V_D}{\Delta I_D} \Big|_{\text{pt. to pt.}}$

Let

$$\Delta V_D = (0.8 - 0.7) \text{ V}$$

$$\Delta I_D = (5 - 0) \text{ mA}$$

$$= \frac{0.8 - 0.7}{(5 - 0) \text{ m}} \Omega$$

$$= \frac{0.1}{5 \text{ m}} = 0.02 \text{ k}\Omega$$

$$= 20 \Omega$$

② In part a the resistance is  $20 \Omega$  which is negligible for the resistive elements is typically in kilohms magnitude.



## Exercise 19

② From the figure 3.13(a) when  $V_{CE} = 6V$  and  $I_C = 2mA$

$I_B$  will be  $18\mu A$  approximately

Here  
 $V_{CE} = 6V$   
 $I_C = 2mA$

## Exercise 19

② From the figure 3.13(a) when  $V_{CE} = 6V$  and  $I_C = 2mA$  then the  $I_B$  approximately  $18\mu A$

Here,

$V_{CE} = 6V$   
 $I_C = 2mA$

Now,

$$\beta_{dc} = \frac{I_C}{I_B} = \frac{2m}{18\mu} = 500 \text{ or } 11.1$$

⑥ We know,

$$\alpha = \frac{\beta}{\beta + 1} = \frac{11.1}{11.1 + 1} = 0.991$$

⑦ We know,

$$I_{CEO} = \beta I_{CBO}$$

Here,  
 $V_{CE} = 6V$

$$\Rightarrow I_{CBO} = \beta (1 - \alpha) I_C \text{ when } I_B = 0$$

$\rightarrow 1 \text{ cell} = 2 \text{ unit}$

$$\Rightarrow I_{CBO} = 11.1 \times (1 - 0.991) \times (0.171) \text{ [from figure 3.13(a)]}$$

when  $V_{CE} = 6V$

and  $I_B = 0mA$

$$\therefore I_{CBO} = 0.171 \text{ mA } 0.34$$

⑧ We know

$$I_{CEO} = \beta I_{CBO}$$

$$\Rightarrow I_{CBO} = \frac{I_{CEO}}{\beta} = \frac{0.34m}{11.1} = 1.52 \mu A \text{ } 3.06 \mu A$$

## Exercise 26

Now,

$$\begin{aligned} V_o &= V_i - V_{be} \\ &= (2 - 0.1) = 1.9 \text{ V} \end{aligned}$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{1.9}{2} = 0.95$$

$$\begin{aligned} \therefore \text{Emitter } I_E &= \frac{V_E}{R_E} = \frac{1.9}{1\text{K}} \\ &= 1.9 \text{ mA} \end{aligned}$$

Here

$$V_{be} = 0.1 \text{ V}$$

$$R_E = 1\text{K} \Omega$$

$$V_i = 2 \text{ V}$$